

Exp 01

Q

EEA-2970

GROUP NO.	03
CLASS S.NO.	14
SECTION	A2 MB
NAME	Pranay Singh

EXPERIMENT NO.: 07

OBJECT: Speed control of wound rotor (slip ring) induction motor by rotor resistance variation

DATE OF PERFORMING THE EXPERIMENT: 10/04/23

DATE OF SUBMISSION OF REPORT: 17/04/23

OTHER GROUP PARTNERS:

CLASS S.NO.	NAME
12	Aragon Pathak
13	Laksh Gupta
15	Md. Ahsan
16	Prakhar Sahu


REMARK (If any by the teacher concerned):

OBJECT: Speed control of a wound rotor (slip rings) using induction motor using rotor resistance variation.

Apparatus Used:

S.No.	Instrument Name	Specification	Make
1.	Voltmeter	0-150 V	EM2V 3B Broad Heath England
2.	Ammeter	0-5 A	EM2A 82 (Bajaj) Model colour
3.	A.C. Motor	420 V	Siemens
4.	D.C. Generator	220 V, 3.8 A	MG - Electric works

Circuit Diagram:

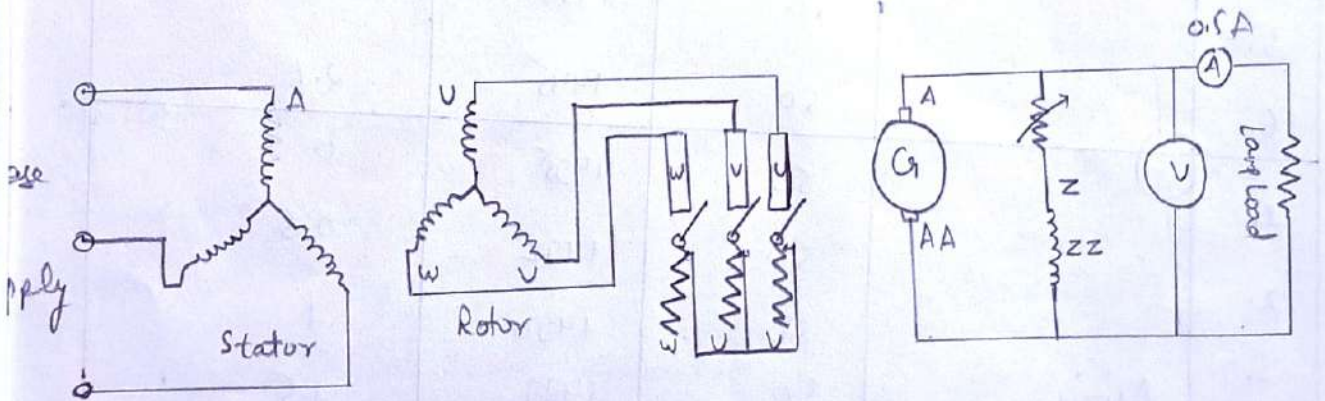

Observation table:

S.No.	Motor Resistance (Step)	Frequency (Hz)	Speed of Motor (rpm)	Load Current of DC Generator (A)
1.	Maximum	50	1457	0
2.		50	1435	0.5
3.		50	1409	1
4.		50	1381	1.5
5.		50	1346	2.1
1.	Medium	50	1491	0
2.		50	1473	0.5
3.		50	1470	1
4.		50	1464	1.5
5.		50	1455	2.1
6.	Minimum	50	1445	2.6
1.		50	1495	0
2.		50	1492	0.5
3.		50	1490	1
4.		50	1487	1.5
5.		50	1485	2.1
6.		50	1483	2.65
7.		50	1480	3.2

Simple Calculation

Low resistance: Reading ④

No. of loads = 3, Speed of Motor = 1487 rpm
frequency = 50 Hz, No. of poles = 4

$$\text{Synchronous speed } (N_s) = \frac{120 \times f}{P} = \frac{120 \times 50}{4} = 1500 \text{ rpm}$$

$$\text{Slip speed of Motor } (s) = \frac{N_s - N}{N_s} \Rightarrow \frac{1500 - 1487}{1500} = 0.0086$$

Output voltage of generator (V_o) = 110 V

Output current of generator (I_o) = 1.5 A

Output power of generator = $V_o \times I_o$

$$P_o = 110 \times 1.5$$

$$P_o = 165 \text{ W}$$

Efficiency of generator (η_g) = 0.85

$\therefore$ Input power of generator = Output power of motor (Induction)

$$\eta_g = \frac{\text{Output Power of generator}}{\text{Input power of generator}} = \frac{P_o}{P_i}$$

$$P_i = \frac{P_o}{\eta_g} = \frac{165}{0.85} = 194.12 \text{ W}$$

Angular speed of Motor (ω) = $\frac{2\pi N}{60}$ rad/sec


$$\omega = \frac{2\pi \times 1487}{60} = 155.72 \text{ rad/s}$$

Output Torque of Induction Motor (T) = $\frac{P_{out}}{\omega}$
 $= \frac{194.12}{156.72} = 1.24 \text{ N-m} [P_g = P_{out}]$

Result Table:

Freq. of 3 phase supply = 50 Hz
 Synchronous speed $N_s = 1500 \text{ rpm}$

Sl. No.	Minimum Resistance		Medium Resistance		Max Resistance	
	Angular Speed (ω)	Torque T (N-m)	Angular Speed (ω)	Torque T (N-m)	Angular Speed (ω)	Torque T (N-m)
1.	156.55	0	155.08	0	152.57	0
2.	156.24	0.414	154.25	0.42	150.27	0.43
3.	155.95	0.829	153.93	0.84	147.55	0.87
4.	155.72	1.24	153.31	1.26	144.62	1.34
5.	155.51	1.75	152.36	1.78	140.95	1.93
6.	155.30	2.21	151.32	2.23		
7.	154.98	2.67				

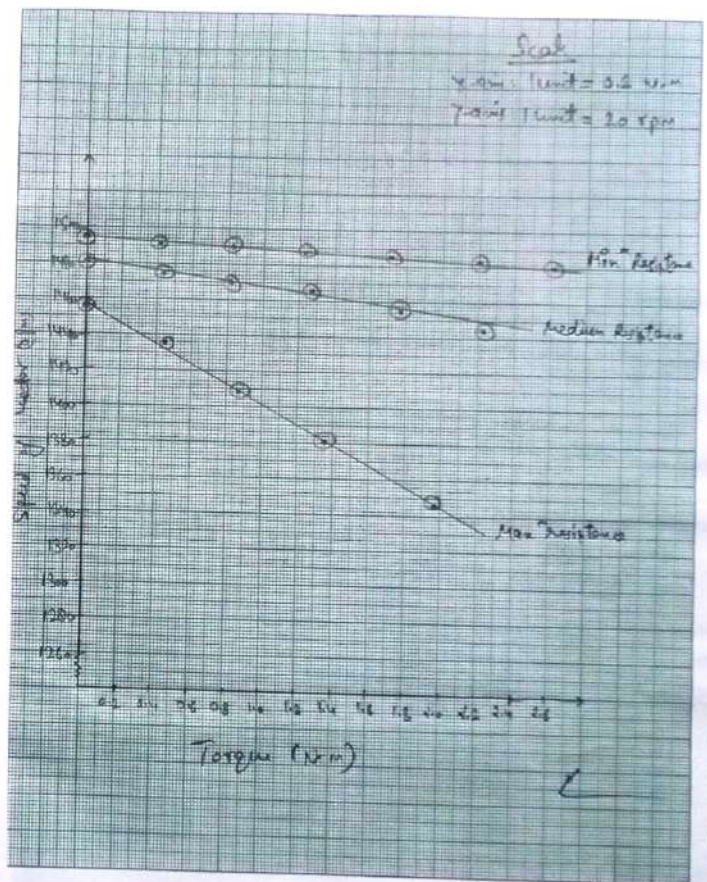

Discussion:

Q1 Discuss methods of speed control of sphere induction motor.

Ans: (i) Speed of a 3 phase induction motor can be considered by these methods $\Rightarrow$

- 1) Stator voltage control: By adding resistance or inductances in the stator circuit, we can change the speed of an induction motor. We can also use an auto-management b/w supply lines and stator of the motor.
- 2) Polar resistance control: By adding resistance in rotor circuit, we can control the speed of the induction motor. This method is popular in control due to its lower cost and energy method.
- 3) By changing pole: As we know, synchronous speed of a motor is inversely proportional to the no. of pole of the stator windings, so by changing poles we can control the speed of a motor.
- 4) Supply frequency control: As we know, synchronous speed of a motor is directly proportional to the supply frequency. Hence we can change the speed of a motor by changing its supply frequency.

EXP-02

ELECTRICAL TECHNOLOGY LAB

(6)
R
11/4/23

Late

NAME - PRANAY SINGH

F.No. - 21MEB448 - 12MB-14

E.No. - GL2254

Course No. - EEA 2970

Date of Experiment - 17/04/23


Date of Submission - 01/05/23

Object - To determine the efficiency V_x load, speed V_x load, & torque V_x load characteristics of a d.c. series motor.

Object: To determine the efficiency vs load, speed vs load & torque vs load characteristics of a d.c. series motor and predict the speed, torque characteristics.

Apparatus Used:

S.No.	Equipment Used	Range	Make
1.	Voltmeter	0-300 V	F.G. England
2.	D.C. Motor	960 rpm, 12.5 A	Made in Great Britain
3.	Pitch Balance	$T_1 = 100 \text{ kgf}$, $T_2 = 50 \text{ kgf}$	-
4.	Ammeter	0-15 A	Automatic Ltd.
5.	Tachometer	-	-

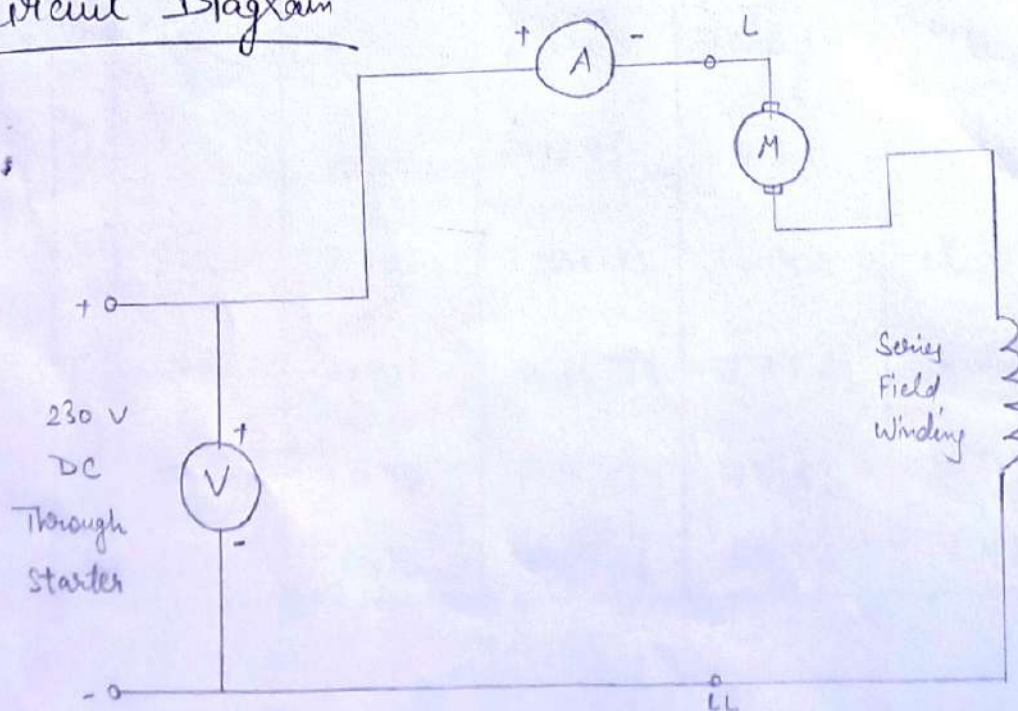Circuit Diagram

Observation table:

S.No.	V (Volt)	I (Amp)	T_1 (kgf)	T_2 (kgf)	N (rpm)
1.	230	12.5	37	8	954
2.		12	34	7	1024
3.		11	30	6	1064
4.		10	26	5.5	1126
5.		9	22	5	1208
6.		8	18	4	1322
7.		7	13	3	1486

Sample Calculation

For reading No ③ $\rightarrow I = 11 \text{ A}$, $V = 230 \text{ V}$, $T_1 = 30 \text{ kgf}$, $T_2 = 6 \text{ kgf}$,
 $N = 1064 \text{ rpm}$

i) Input Power, $P_{in} = VI = 230 \times 11 = 2530 \text{ W}$

ii) Output Power, $P_{out} = \frac{2\pi N(T_1 - T_2)R_g}{60} = \frac{2\pi \times 1064(30 - 6) \times 0.0762 \times 9.8}{60}$
 $= 1996.93 \text{ W}$

iii) Efficiency $= \frac{\text{Output}}{\text{Input}} \times 100\% = \frac{1996.93}{2530} \times 100 = 78.93\%$

iv) Torque developed $= (T_1 - T_2)R_g = 24 \times 0.0762 \times 9.8$
 $= 17.92 \text{ Nm}$

Result table:

S.No.	Current (A)	Input Power (W)	Output Power (W)	Efficiency (%)	Torque (Nm)	Voltage (V)
1.	12.5	2875	2163.49	75.25	21.65	230
2.	12	2760	2162.08	78.34	20.16	230
3.	11	2530	1996.93	78.93	17.92	230
4.	10	2300	1805.11	78.49	15.31	230
5.	9	2070	1605.92	77.58	12.69	230
6.	8	1840	1447.34	78.66	10.45	230
7.	7	1610	1162.06	72.17	7.46	230

Discussion

Q1 Why do the dc series motor gives high starting torque?

Ans. DC series motor are widely used for the purpose requiring high starting torque like in cranes, electric traction, etc.
For any d.c. motor, torque is directly proportional to the flux and armature current i.e., $T = K_a \phi I_a$ (1) where K_a - constant
 ϕ - flux


In case of dc series motor, the flux produced is directly proportional to the armature current. Hence torque is directly proportional to the square of armature current.

Therefore, $\phi = C I_a$ where C - constant

Then, $T = K_a C I_a^2$ (2) $K = K_a C$

As we know that the max^m permissible current at starting of DC motor is limited about 1.5 times that of rated current. Thus, loads requiring high starting torque such as cranes, traction types.

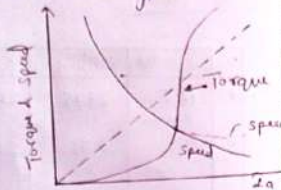This is clear that higher the armature or load current, higher is the torque till the magnetic flux causes saturation. Once saturation occurs, the flux will no longer increase in proportion to the increment in current and thus limits the increase in torque.




Q2 Mention industrial applications of dc series motor.


Ans. Some applications where d.c. motor in industries are

- (i) DC series motor are widely used for electrical traction applications i.e., these motors are widely used in electric locomotives, rapid transit system and trolley cars.
- (ii) DC series motor are employed in cranes, hoist and in cars because of high starting torque capability.


Efficiency Vs Current

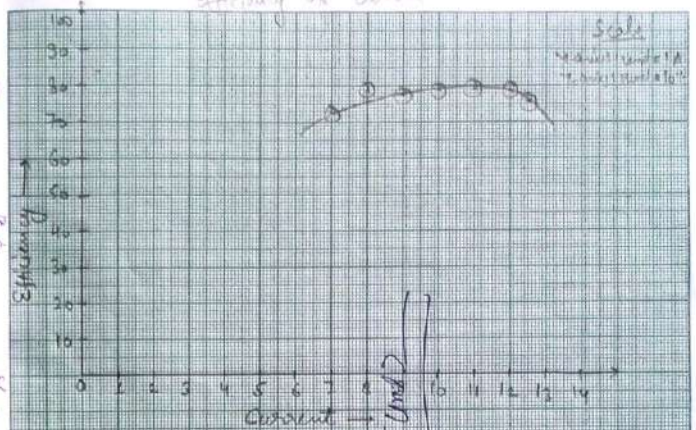


Torque Vs Speed

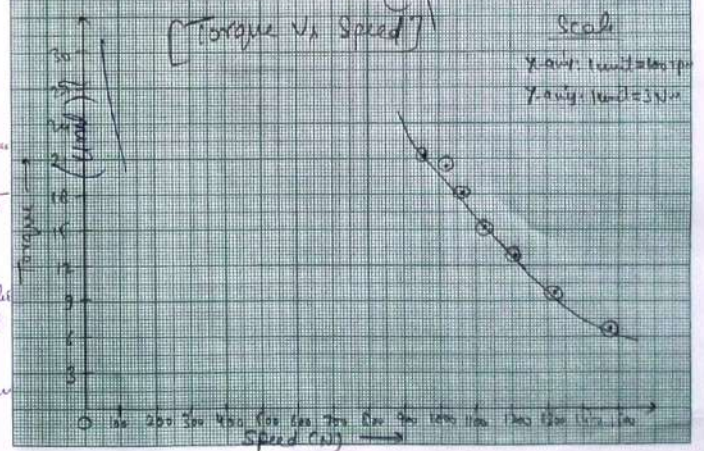

Speed Vs Current

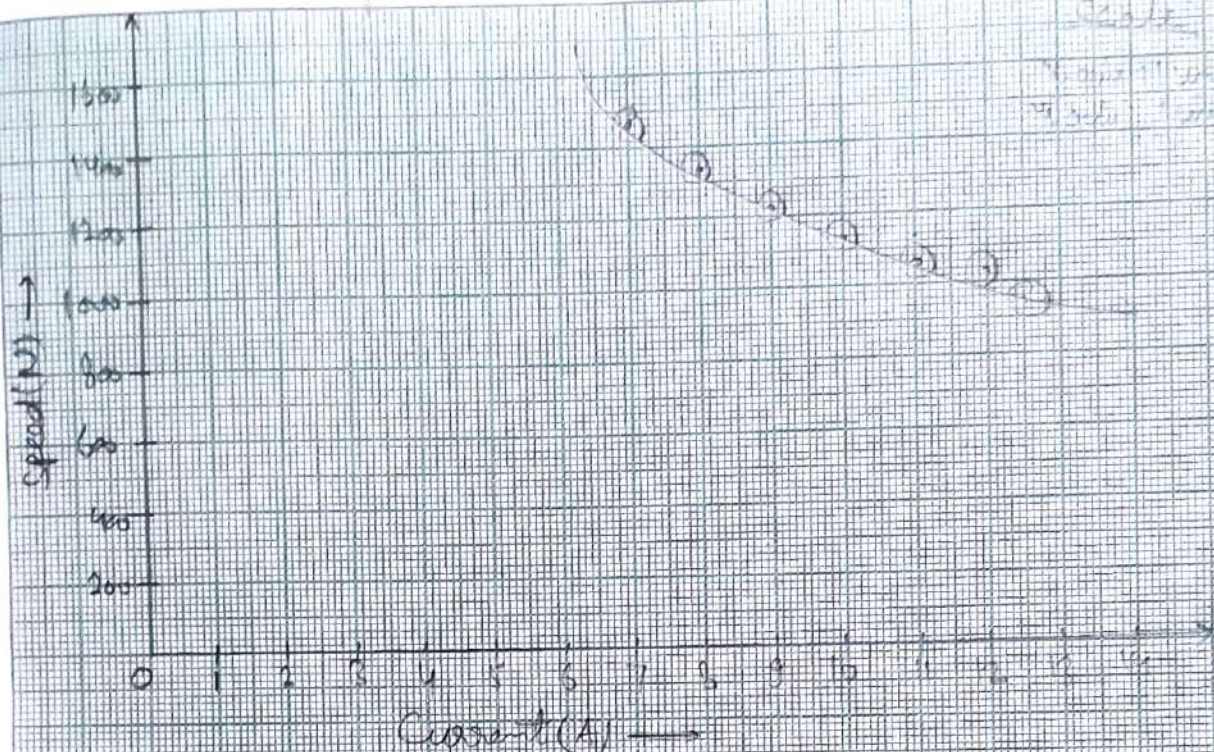

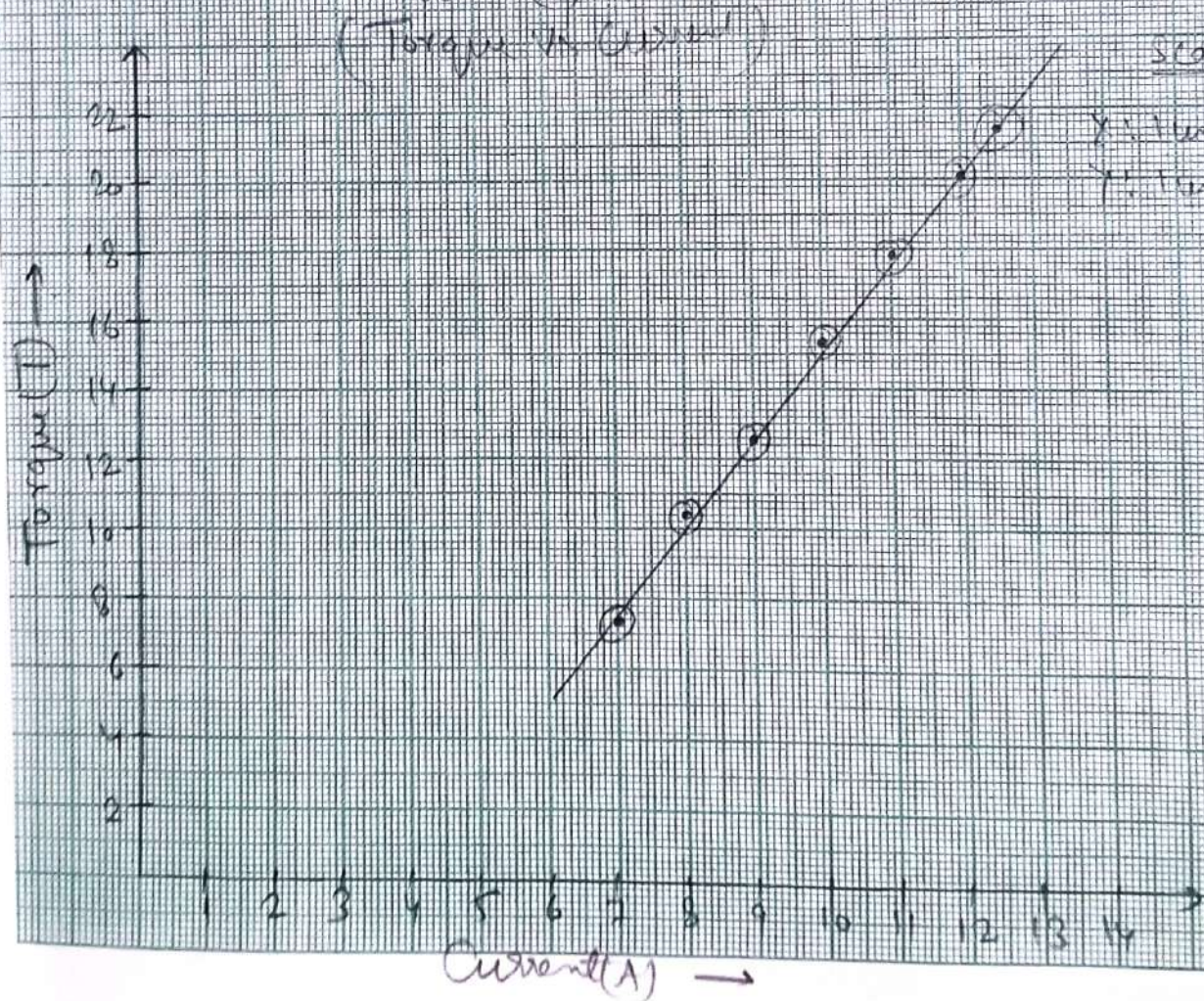Scale
 X: 1 unit = 1 A
 Y: 1 unit = 200 N



Scale
 X: 1 unit = 1 A
 Y: 1 unit = 2 N

Ep-3

Department of Mechanical Engg.

Zakir Hussain College of Engineering And Technology

AMU, Aligarh

LAB REPORT

Name : PRANAY SINGH

Class : A2MB

Faculty No. : 21MEB448

Serial no. : 14

Enroll No. : GL2254

Course Title : Electrical Technology Lab

Course No : EEA 2970

Brief Objective : Determination of speed load and efficiency
load characteristics of a d.c. shunt and compound motor

Date of Experiment Performed : 06/02/2023

Date of Submission : 13/02/2023


Teacher's Remark :

Experiment -1

Name - Pranay Singh
F.No. - 21ME8448
S.No. - 14(A2MB)

SUBJECT: Determination of speed load and efficiency load characteristics of a d.c. shunt and compound motor. :-

Circuit Diagram :

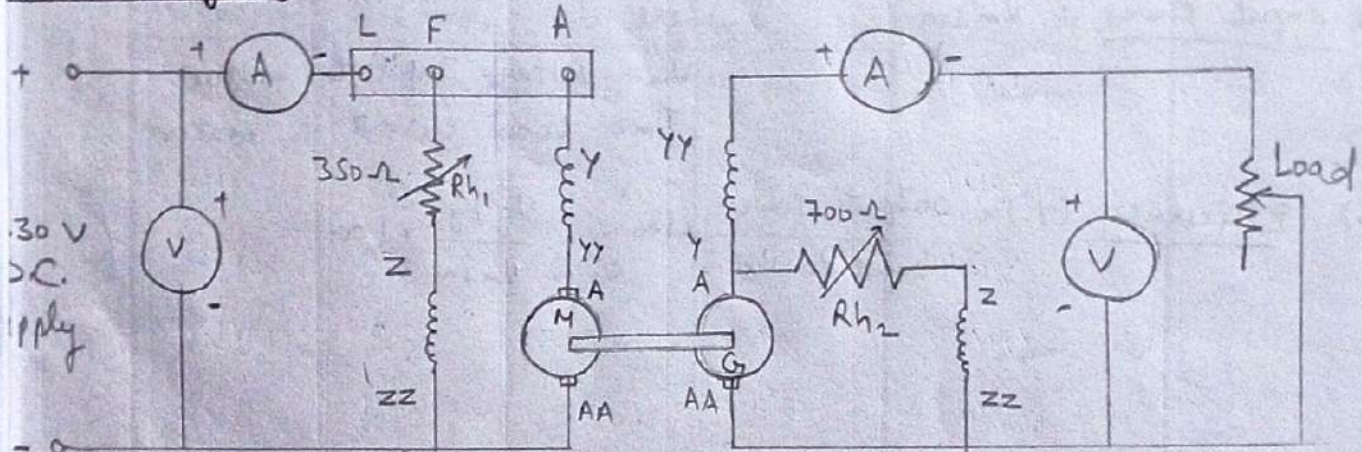

Differentially/ Cumulatively Compounded D.C. Motor.

Apparatus Used:

S.No.	Equipment Name	Range	Make
1.	Voltmeter	0-300 V	Automatic Lt. India
2.	Ammeter	0-15 A	Automatic Lt. India
3.	Rheostat	430 Ω , 2 A	British Electric Lt.
4.	Wires	—	India
5.	D.C. Motor	1450 rpm / 230v	Bombay
6.	D.C. Generator	1450 rpm / 253v	Bombay
7.	Bulb	150 watt	Mysore

Formula Used:

(1) Output Power = $V_g I_g$

where,

V_g = Voltage input to generator
 I_g = Load current to generator

(2) Input Power = $V_m I_m$

where,

V_m = Voltage input to motor
 I_m = Load current to motor

(3) Efficiency (%) = $\frac{\text{Output Power}}{\text{Input Power}} \times 100 = \frac{V_g I_g}{V_m I_m} \times 100$

OBSERVATION TABLE:

Cumulatively Compounded D.C. Motor

S.No.	Input to Motor		Output from generator		Speed (RPM)
	V (Volts)	I (Amp)	V	I	
1.	246	3.2	230	0	1600
2.	246	4.4	230	1.3	1587
3.	246	5.6	230	2.6	1572
4.	246	6.9	230	3.8	1560
5.	246	10.2	230	6.8	1541
6.	246	11.8	230	8	1532

Differentially Compounded D.C. Motor

S.No.	Input to Motor		Output from generator		Speed (RPM)
	V	I	V	I	
1.	240	3.2	230	0	1600
2.	240	4.4	230	1.3	1578
3.	240	5.8	230	2.6	1556
4.	240	7	230	3.8	1536
5.	240	8.2	230	5.1	1516
6.	240	10.2	230	6.8	1494

3. Shunt Compounded D.C. Motor.

SNo.	Input to motor		Output from generator		Speed(RPM)
	V	I	V	I	
1.	240	3.2	230	0	1600
2.	240	5	230	1.3	1581
3.	240	5.8	230	2.6	1565
4.	240	7	230	3.8	1550
5.	240	8.2	230	5.1	1535
6.	240	10.2	230	6.8	1520
	240	12	230	8	1505

Sample Calculation for reading 3:

(Shunt Compounded)

We know output power generator = $V_g I_g = (P_o)_g$

Input power to motor $(P_i)_m = V_m I_m$

Input power to generator $(P_i)_g =$ Output power from motor $(P_o)_m$

$$\therefore (P_i)_g = (P_o)_m$$

Efficiency of generator $(\eta)_g = \frac{\text{Output Power } (P_o)_g}{\text{Input Power } (P_i)_g}$

(We assume $\eta = 85\%$)

$$0.85 = \frac{230 \times 2.6}{\text{Input } (P_i)_g}$$

$$(P_i)_g = 703.53 \text{ watt} \quad [(P_i)_g = (P_o)_m]$$

Efficiency of motor $(\eta)_m = \frac{\text{Output Power } (P_o)_m}{\text{Input Power } (P_i)_m}$

$$(\eta)_m = \frac{703.53}{240 \times 5.8} = 0.5054$$

$$(\eta)_m = 50.54\%$$

cumulatively Compounded =>

We know output power generator = $V_g I_g = (P_o)_g$

Input power to motor $(P_i)_m = V_m I_m$

Input power to generator $(P_i)_g =$ output power from motor $(P_o)_m$

$$\therefore (P_i)_g = (P_o)_m$$

Efficiency of generator $(\eta)_g = \frac{\text{Output Power } (P_o)_g}{\text{Input Power } (P_i)_g}$

(We assume $\eta = 85\%$)

$$0.85 = \frac{230 \times 2.6}{\text{Input } (P_i)_g}$$

$$(P_i)_g = 703.53 \text{ watt} \quad [(P_i)_g = (P_o)_m]$$

Efficiency of motor $(\eta)_m = \frac{\text{Output Power } (P_o)_m}{\text{Input Power } (P_i)_m}$

$$(\eta)_m = \frac{703.53}{240 \times 5.8} = 0.5106$$

$$(\eta)_m = 51.06\%$$

Differentially Compounded D.C. Motor

We know output power generator = $V_g I_g = (P_o)_g$

Input power to motor $(P_i)_m = V_m I_m$

$\therefore$ Input power to generator $(P_i)_g =$ output power from motor $(P_o)_m$

$$\therefore (P_i)_g = (P_o)_m$$

$$\text{Efficiency of generator } (\eta)_g = \frac{\text{output Power } (P_o)_g}{\text{Input Power } (P_i)_g}$$

(We assume $\eta = 85\%$)

$$0.85 = \frac{2367.21}{\text{Input } (P_i)_g}$$

$$(P_i)_g = 703.53 \text{ watt} \quad [(P_i)_g = (P_o)_m]$$

$$\text{Efficiency of motor } (\eta)_m = \frac{\text{Output Power } (P_o)_m}{\text{Input Power } (P_i)_m}$$

$$(\eta)_m = \frac{703.53}{240 \times 5.8} = 0.5054$$

$$(\eta)_m = 50.54\%$$

Result table: Shunt Compound

Power input to motor (watt)	Power output from motor (watt)	Efficiency of motor $(\eta)_m$	Speed (rpm)
768	0	0	1600
1200	351.76	29.31%	1581
1392	703.53	50.54%	1565
1680	1028.24	61.2%	1550
1968	1380	70.12%	1535
2448	1840	75.16%	1520


Differentially Compounded

Power input to motor (watt)	Power output from motor (watt)	Efficiency of motor $(\eta)_m$	Speed (rpm)
768	0	0	1600
1056	351.76	33.31%	1578
1392	703.53	50.54%	1556
1680	1028.24	61.21%	1536
1968	1380	70.12%	1516
2448	1840	75.16%	1494

Cumulatively Differentially Compounded

Power input to motor (Watt)	Power output from motor (Watt)	Efficiency of motor (%)	Speed (rpm)
727.2	0	0	1600
1082.4	351.76	32.49 %	1589
1397.6	703.53	50 %	1572
1697.4	1028.24	60.57 %	1560
2509.2	1840	73.33 %	1541
2902.8	2164.71	74.57 %	1532


Discussion :

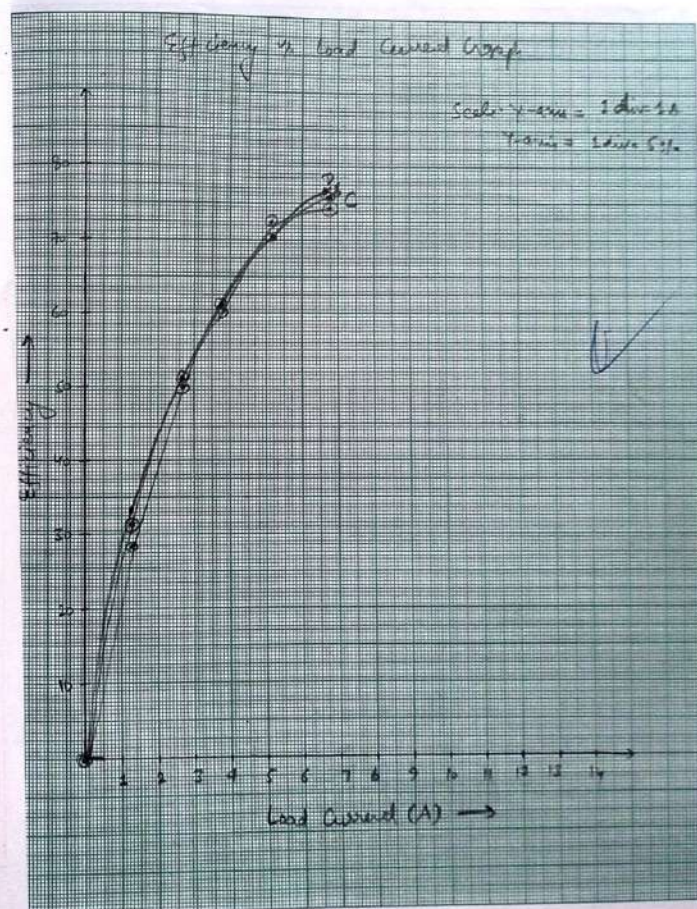

Speed vs Load Current Graph

Scale on axis = 1 div = 1 A

1 cm = 1 div = 10 rpm

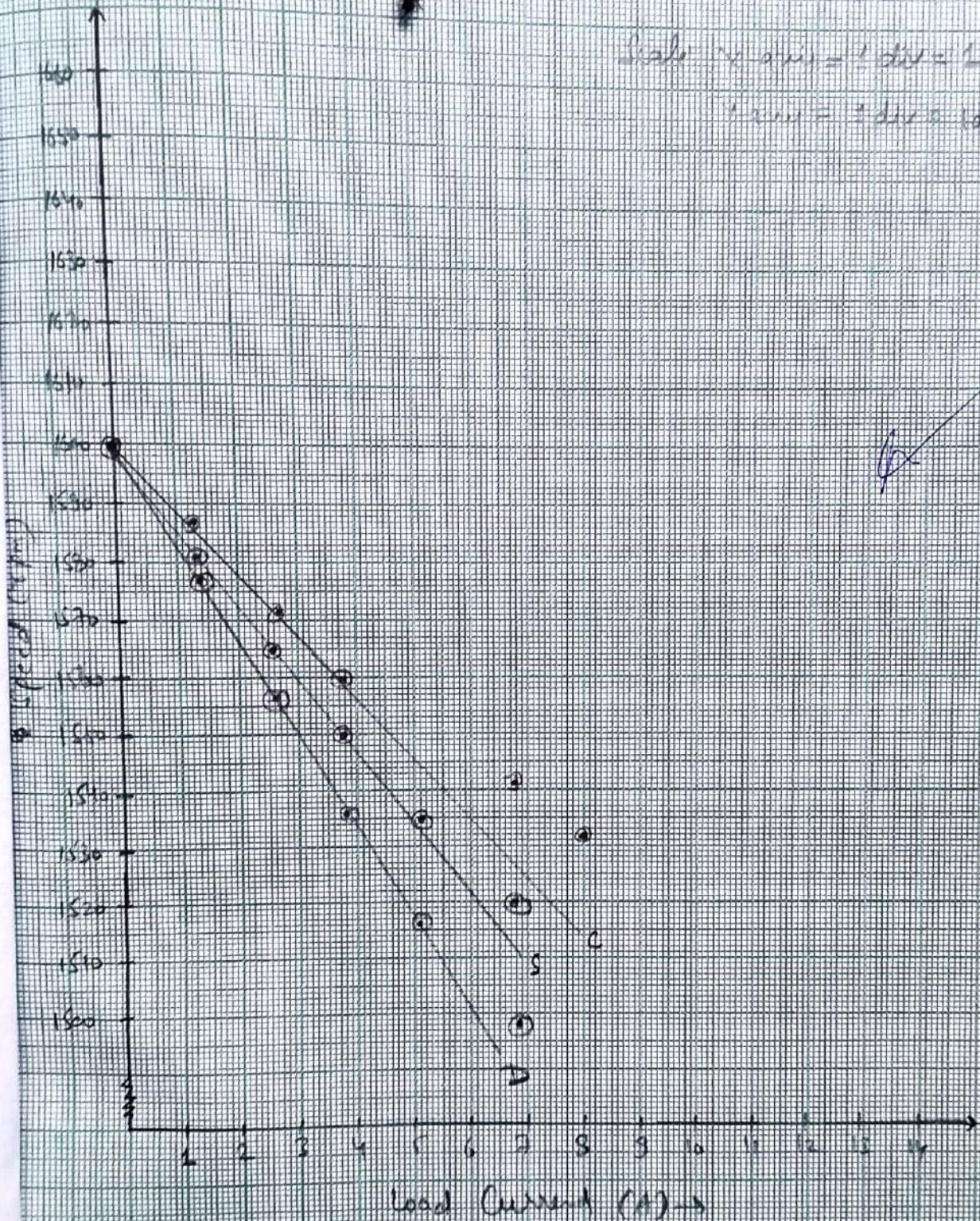


Discussion :

1) Explain why dc shunt motors are regarded as constant speed motors. Mention industrial applications of shunt motors.

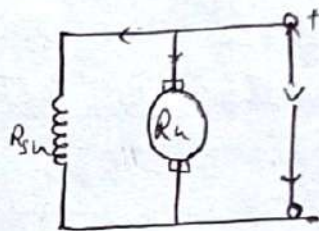2) In a DC shunt motor, speed is directly proportional to the voltage across the armature terminals and inversely proportional to the flux (ϕ) due to the field windings ($N \propto \frac{1}{\phi}$)
i.e. $N \propto \frac{1}{I_{sh}}$.

In a shunt motor, the shunt field current, I_{sh} is always constant since the field winding is connected in parallel to the armature winding and the supply voltage.



Under a constant supply voltage and normal load, the field flux in a shunt motor remains approximately the same.

The flux decreases due to the armature reaction is negligible under normal condition.

If load change is not considered since a DC shunt motor has a constant flux ϕ and a constant supply voltage, the speed of the motor remains constant.

This is the reason why, DC shunt motors are regarded as constant speed motors.

Shunt DC motors are utilized in Centrifugal Pumps, Lifts, Weaving machines, Lathe machines, Blowers, fans, Conveyors, Spinning machines, and other applications where a consistent speed is required.

Ep-4

8A
12/2/24

EEA-2970

GROUP NO.	03
CLASS S.NO.	14
SECTION	A2MB
NAME	PRANAY SINGH

EXPERIMENT NO.: 02 ~~01~~

OBJECT: Determination of characteristics of 3 phase induction motor by load test.

DATE OF PERFORMING THE EXPERIMENT: 13/02/23

DATE OF SUBMISSION OF REPORT: 20/02/23

OTHER GROUP PARTNERS:

CLASS S.NO.	NAME
12	Crageen Pathak
13	Laksh Gupta
15	Moh. Akham
16	Prakhar Sahu


REMARK (If any by the teacher concerned):

Experiment - 2

Name - Pranay Singh
S.No - 14 (A2MB)
F.No - 21MEB448

Object: Determination of characteristics of 3 phase induction motor by load test.

Circuit Diagram:

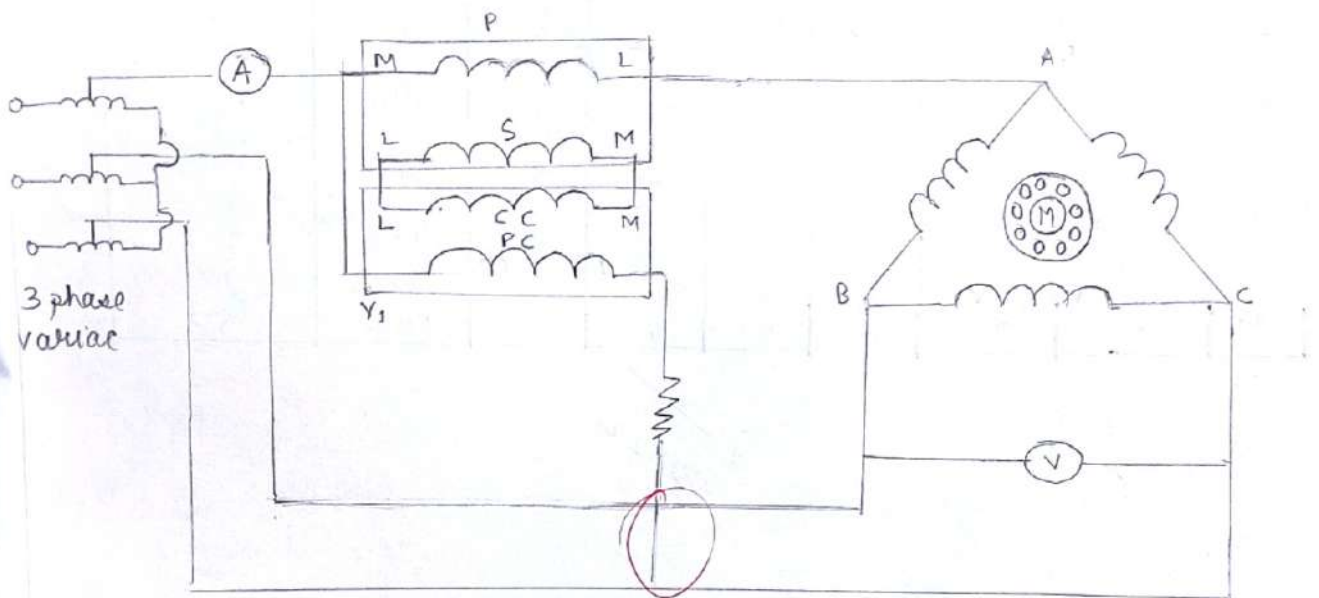

circuit diagram for load test on 3 phase induction motor.

Apparatus Used:

S.No.	Equipment Name	Range	Make
1.	Ammeter	0-15 A	Holand
2.	Voltmeter	0-300 V	-
3.	Induction motor with balance	950 rpm, 230V, 14A 100 kgf, 50 kgf	Bombay
4.	Current transformer		Bombay
5.	Wattmeter	0-300 W	Automatic Electric Ltd.
6.	Pressure Coil	-	-

Observation table:

S.No.	Voltage (V)	Current (A)	Wattmeter Reading (Watt)		Tension (kgf)		Speed (N) rpm	Frequency (Hz)
			W_1	W_2	T_1	T_2		
1.	230	14	135	70	60	12	948	50
2.	230	13	180	50	52	11	951	50
3.	230	12	160	45	45	10	962	50
4.	230	11	150	30	40	9	970	50
5.	230	10	140	20	35	8	975	50
6.	230	9	120	10	26	6	982	50
7.	230	8	90	-10	12	3	992	50
8.	230	7	70	-40	0	0	1000	50

2
13/12/22

Formula used:

$$\text{Torque} = (T_1 - T_2) \left(\frac{D}{2} \right) g \quad \text{N-m}$$

$$\text{Input Power} = W_1 + W_2$$

$$\text{Output Power} = \frac{2\pi N \times \text{Torque}}{60 \times \text{M.F.} \times \text{W.F.}}$$

where, T_1, T_2 → Tension in belt
 D → Diameter of Pulley (6 inch = 0.1524 m)
 W_1, W_2 → Reading of wattmeter
 N → Speed rpm
 M.F. → Multiplying factor
 W.F. → Wattmeter factor
 $\text{Factor} = \text{M.F.} \times \text{W.F.} = 4 \times 4 = 16$

Sample Calculations:

For Reading 3:

$$T_1 = 45 \text{ kgf}, T_2 = 10 \text{ kgf}, W_1 = 160 \text{ W}, W_2 = 45 \text{ W}, N = 962 \text{ rpm}$$

$$\text{Torque} = (T_1 - T_2) \left(\frac{D}{2} \right) g = (45 - 10) \left(\frac{0.1524}{2} \right) \times 9.8 = 26.14 \text{ N-m}$$

$$\text{Output Power} = \frac{2\pi N T}{60 \times \text{Factor}} = \frac{2 \times \pi \times 962 \times 26.14}{60 \times 16} = 164.58 \text{ W}$$

$$\text{Input Power} = W_1 + W_2 = 160 + 45 = 205 \text{ W}$$

$$\text{Efficiency } (\eta) = \frac{\text{Output P}}{\text{Input P}} = \frac{164.58}{205} \times 100 = 80.3 \%$$


Result Table:

S.No.	Voltage (V)	Current (A)	Speed (N) rpm	Input Power (Watt)	Torque N-m	Output Power (Watt)	% Efficiency
1	230	14	948	265	35.84	222.37	83.91%
2	230	13	951	230	30.62	190.58	82.86%
3	230	12	962	205	26.14	164.58	80.28%
4	230	11	970	186	23.15	146.97	78.65%
5	230	10	975	160	20.16	128.65	80.41%
6	230	09	982	130	14.94	96.02	73.86%
7	230	08	992	80	6.72	43.63	54.54%
8	230	07	1000	30	0	0	0%

Discussion: The load test of Induction motor is performed to compare its complete performance i.e. Torque, η , etc. During this test motor is operated at a rated voltage (230V) of approx constant frequency (50Hz) loaded normally on brake belt.

Discussion from graph:

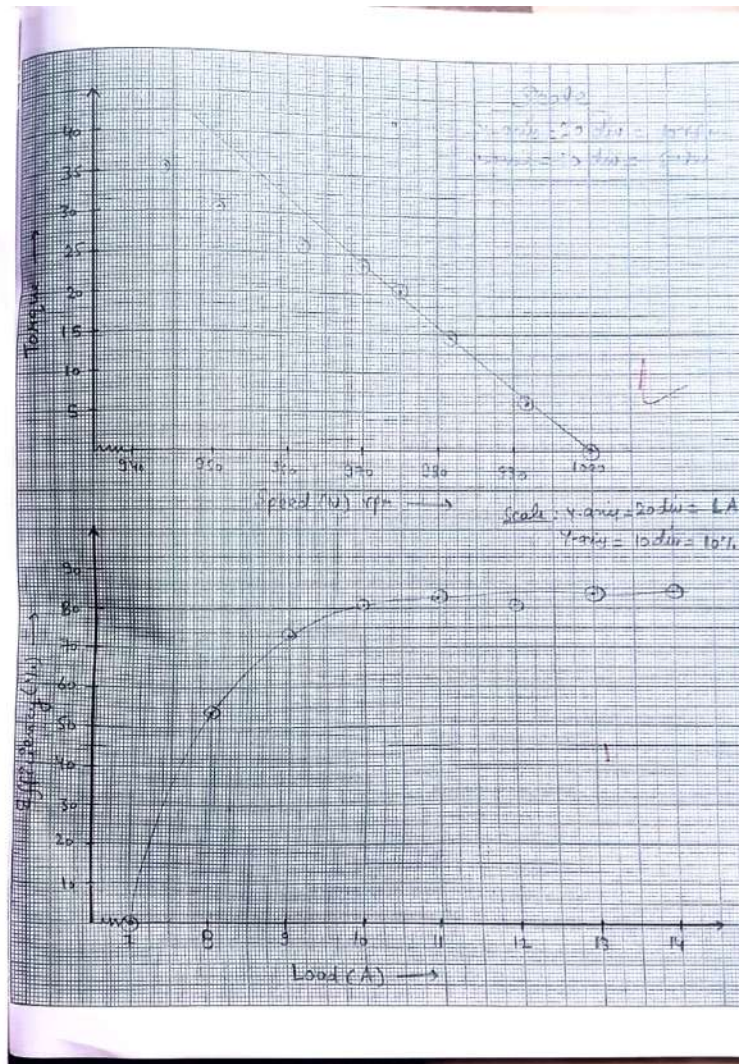
- ① Torque v/s Speed → We can see from the graph that as the speed of the motor increases, the torque decreases.
- ② Efficiency v/s Load → We can see from the graph that as the load current increases, the efficiency also increases.
- ③ Speed v/s Load → We can see from the graph that as the load increases, the speed decreases.



Graph

Motor - C-250 (A)

Y-axis - Speed (rpm)

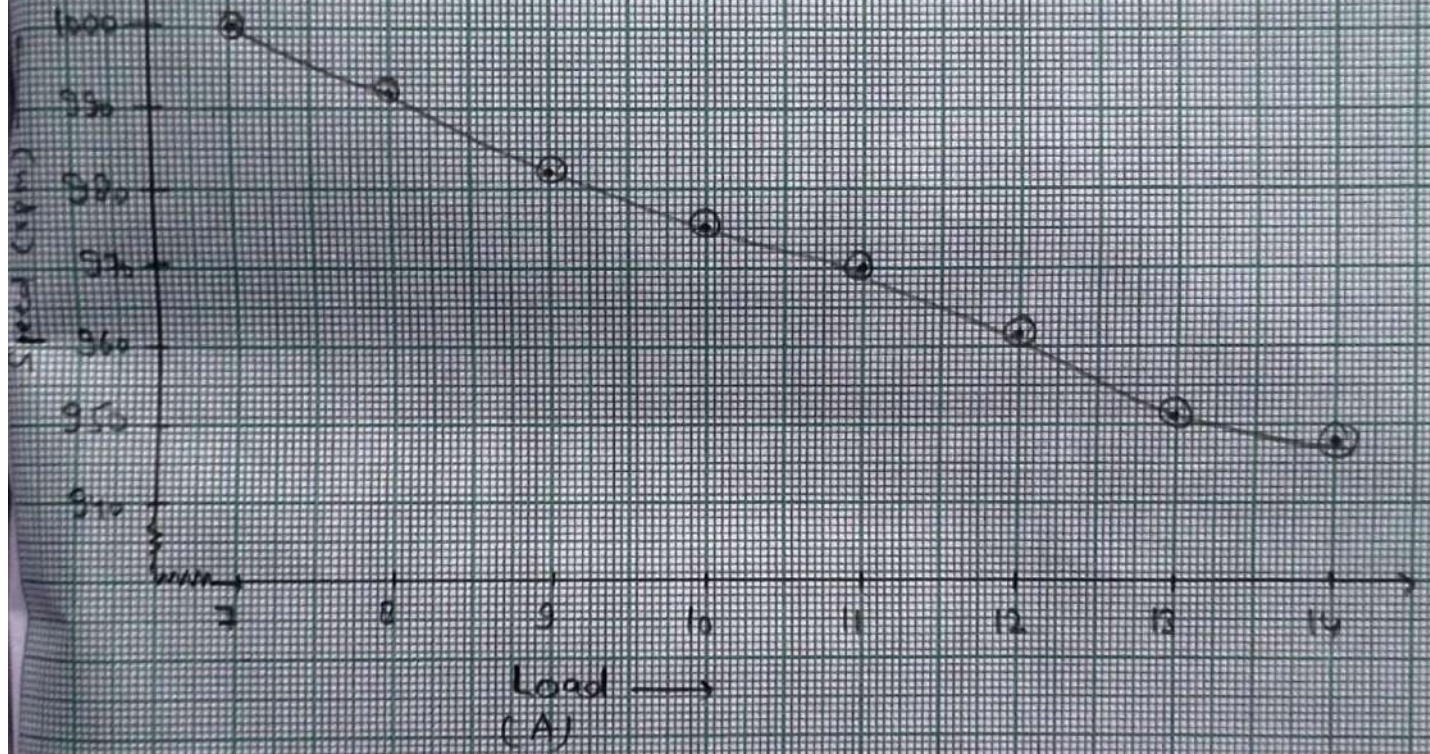

L

Exp-5

⑦
P
1/5/23

EEA-2970

GROUP NO.	03
CLASS S.NO.	14
SECTION	A2MB
NAME	PRANAY SINGH

EXPERIMENT NO.: 05

OBJECT: Static characteristics of an SCR

DATE OF PERFORMING THE EXPERIMENT: 20/02/23

DATE OF SUBMISSION OF REPORT:

OTHER GROUP PARTNERS:

CLASS S.NO.	NAME
12	Cragan Pathok
13	Laksh Gupta
15	Mo. Arham
16	Pratchas Sahu

REMARK (If any by the teacher concerned):

Observation table:

Latching Current = 26 mA

Holding Current = 11 mA


S.No.	Anode Current (mA)	Voltage (V_{AK})
1	25	0.850
2	65	0.844
3	100	0.846
4	150	0.850
5	200	0.860
6	255	0.877
7	305	0.885
8	365	0.896
9	415	0.910
10	455	0.920
11	500	0.930

P
20/2/23

Exp-03

OBJECT: Static characteristics of an SCR

CIRCUIT DIAGRAM:

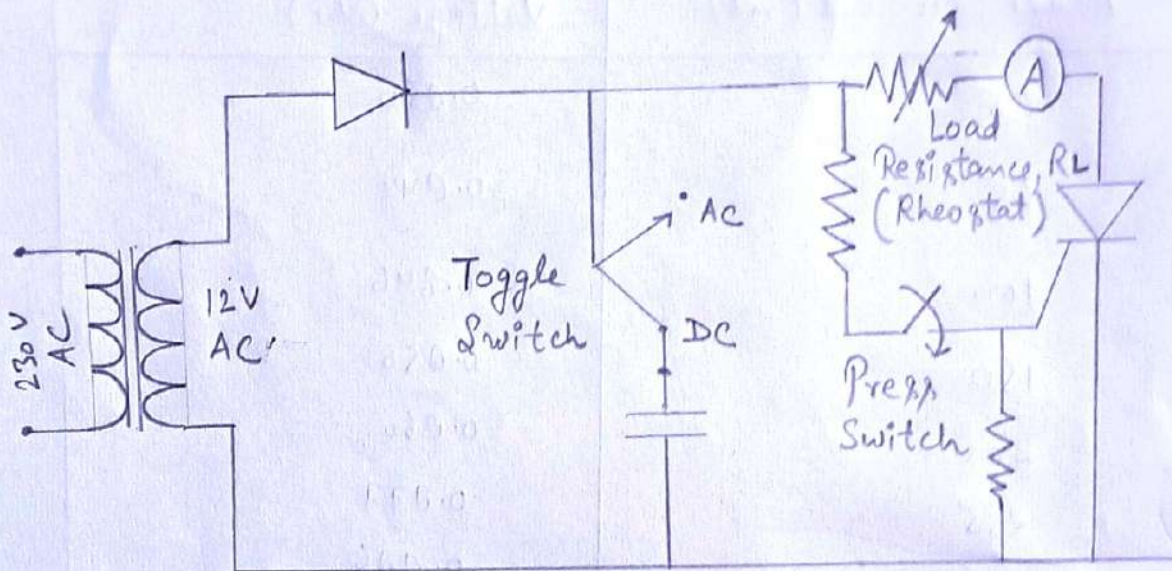

Apparatus Used:

S.No.	Equipment Name	Range	Make
1.	Multimeter (Digital)	0-999V (DC)	Sciencetech
2.	Ammeter (DC)	(i) 0-0.5A (ii) 0-100mA	AE-Limited
3.	Rheostat	1590 Ω , 0.5A	stead
4.	Stepdown transformer	230V to 12V	Delta
5.	SCR		

Q1. Why SCR conducts so long as gate signal is present in a.c. test?


A: This is because with no gate signal applied, a silicon controlled rectifier blocks current in both directions of an AC waveform, and once it is triggered into conduction, the regenerative latching action means that it cannot be turned "OFF" again just by using its Gate.

In case of an SCR we obtain a rectifier AC output due to presence of diode but the voltage becomes zero at the end of each of half wave cycle. Hence it conducts as long as gate signal is present in a.c. test.

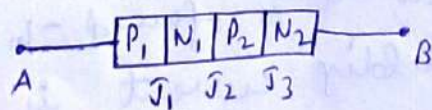Q2. Why SCR fails to maintain conduction below holding current?

A: For turning off the SCR anode current must fall below the holding current. If the anode current is greater than the holding current, SCR fails to turn off even when it is in conducting mode and a reverse voltage is applied between anode and cathode.

SCR fails to conduct below holding current due to reduced current carriers flowing through J^N . J_2 is also reduced current in N_1 of P_2 region, regain their semiconductor properties depletion layer forms across J_2 which is reversed biased and bring back the device to blocking state.



Q3. What are the specifications of SCR used in experiment?

Sol: Experimentally, holding current is found to be 15 mA, but according to specification, the holding current is 40 mA. Thus deviation is of 25 mA.

Specification of SCR

Type No.	$I_{T(RMS)}$ (A)	V_{DRM} (V)	V_{RRM} (V)	V_{RSM} (V)	V_E (V)	V_{GT} (V)	I_{GT} (mA)	T_{SM}
DE 2508	25	800	800	900	1.5	3	40	100

① Conducting State

- Maximum forward voltage drop at $t_j = 25^\circ C$ $V_{tmax} = 2.5 V$
- Average ON state current $I_{T(ON)} = 16 A$
- Holding current DC value $I_H = 40 mA$
- Average ON-state Power dissipation $P_O = 30 W$
- RMS surge (non-repetitive) ON-state Current $P_t = 220 A^2 sec$

② Gate Parameter


- Max^m Gate Triggering Current $I_{GTM} = 60 mA$
- Max^m Gate Triggering voltage $V_{GTM} = 3.5 V$

③ Switching Parameter

- Rate of applied voltage $= 20 V/\mu s$
- Rate of change of ON-state voltage $= 25 A/\mu s$

Ques How much exp. data deviate from specified data?

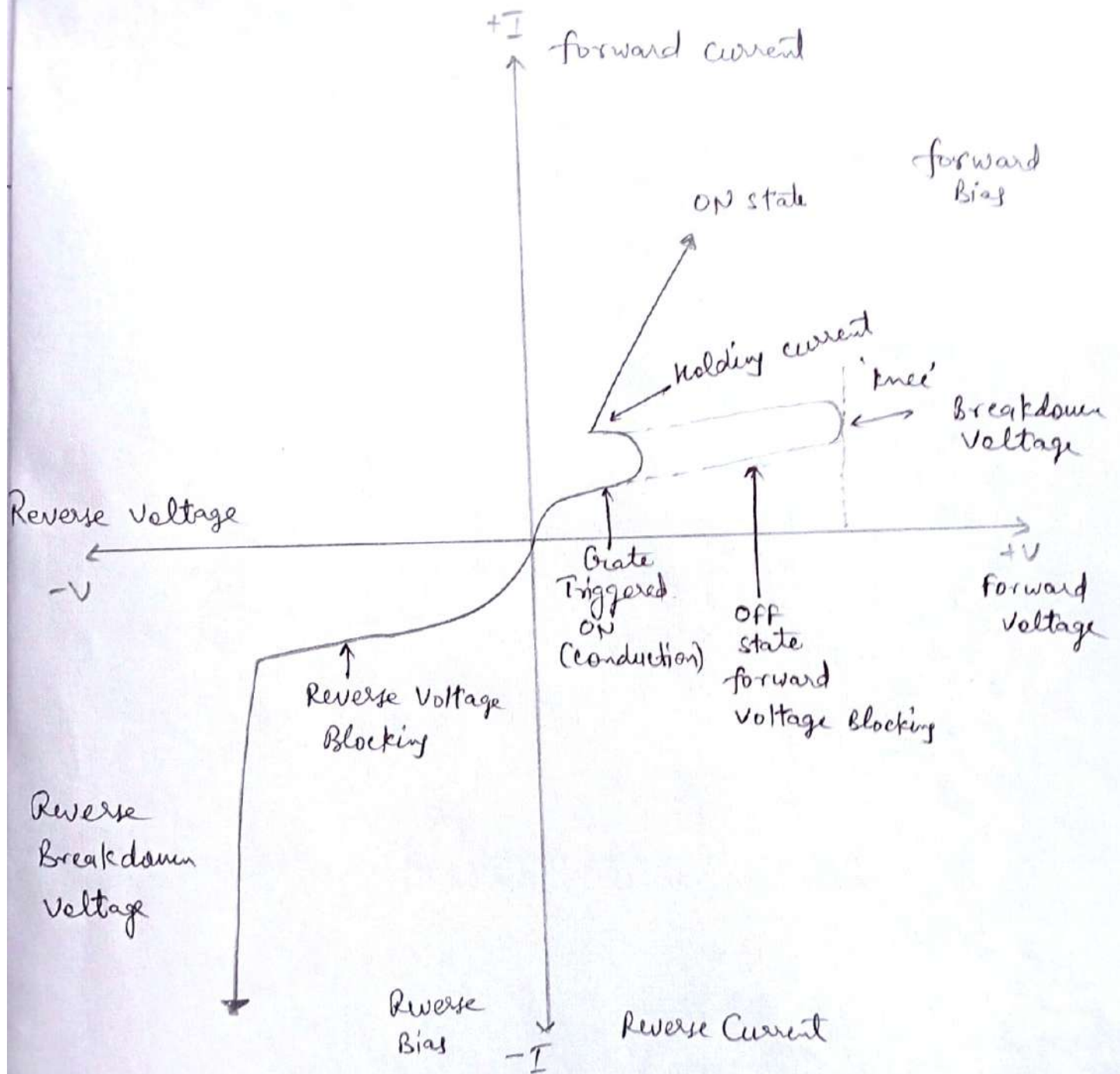Sol: Experimentally holding current is found to be 11 mA but acc. to specification, the holding current is 40 mA. Thus deviation is of 29 mA.




V-I characteristics of an SCR

Scale

Y-axis: Unit = mA

X-axis: Unit = V

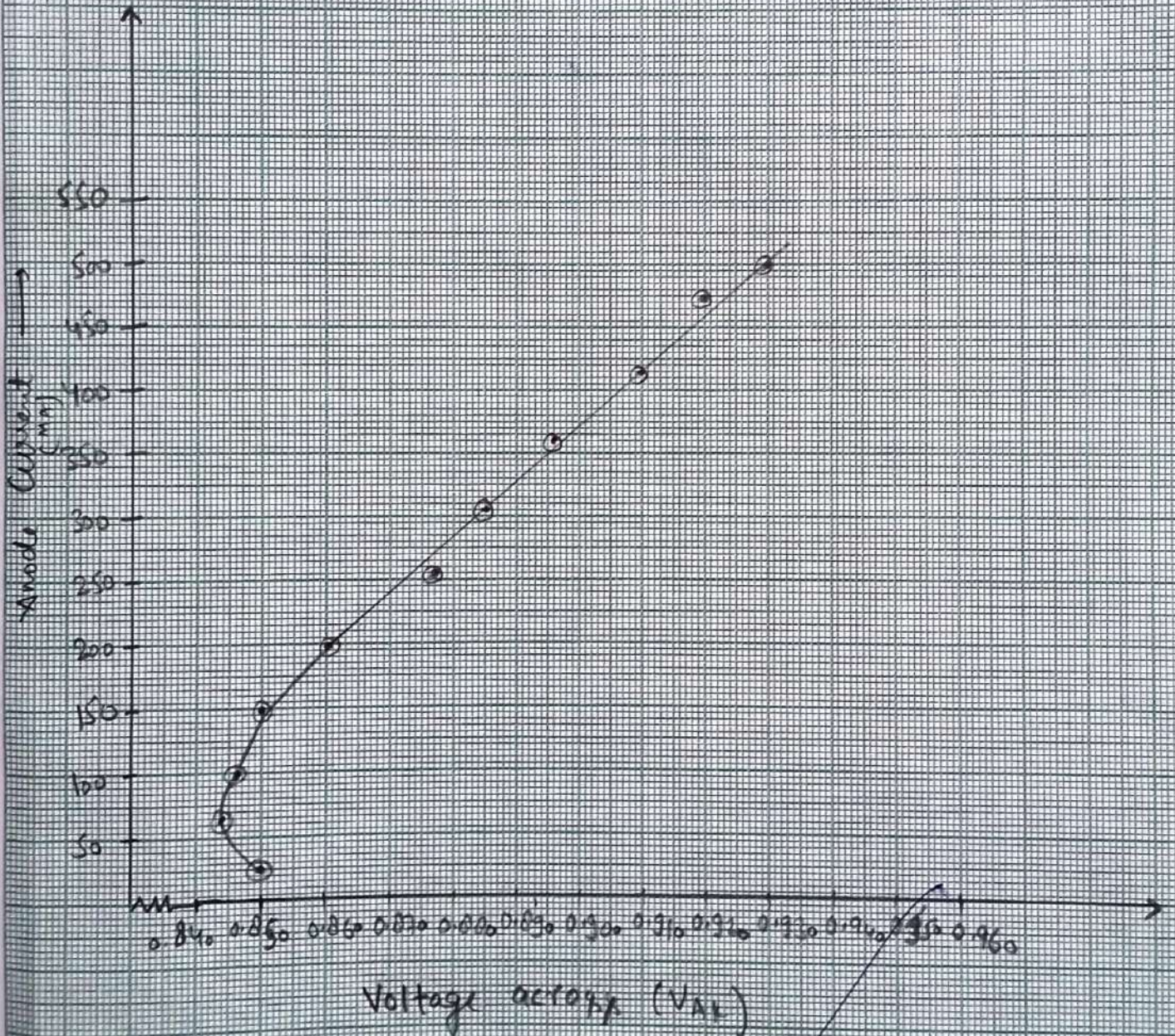

(ant 77)

Exp 06

(8)
P-
27/3/23

EEA-2970

GROUP NO.	03
CLASS S.NO.	14
SECTION	A2MB
NAME	Pranay Singh

EXPERIMENT NO.: 04

OBJECT: TRIAC & AC phase control

DATE OF PERFORMING THE EXPERIMENT: 27/02/2023

DATE OF SUBMISSION OF REPORT:

OTHER GROUP PARTNERS:

CLASS S.NO.	NAME
12	Oragon Pathak
13	Laksh Gupta
15	Mo. Arhem
16	Prakhar Sahu

REMARK (If any by the teacher concerned):


B.T.E.C.T: Triac and a.c. phase control.

- (i) To study a diac based trigger circuit
(ii) To study ac phase controlled switching using a diac and triac

Apparatus used :

S.No.	Equipment Name	Range	Make
1.	Auto Transformer	0-230V, 10A 2.7 kVA	AE
2.	DSO	50 MHz (EDUX1002A)	Keysight
3.	Digital Multimeter	0-1000V (D.C.)	Sciencetech
4.	Bulb	15 W	Crompton
5.	Experimental kit		

Circuit Diagram :

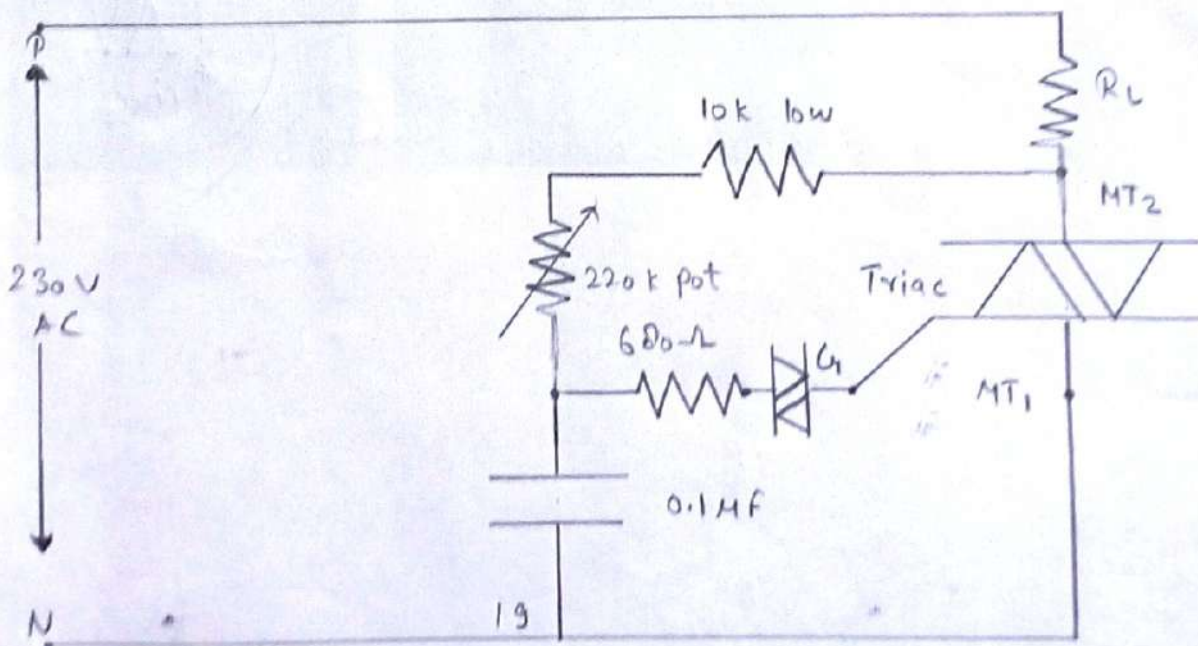


AC Phase Control by triac

OBSERVATION TABLE:



S.No.	Input Voltage (V)	Output Voltage (V)	Firing Angle
1.	230	45.9	$5.5 \times 22.5 = 123.75$
2.	230	94.1	$4.2 \times 22.5 = 94.5$
3.	230	149.6	$3 \times 22.5 = 67.5$
4.	230	192.4	$2 \times 22.5 = 45$
5.	230	210.2	$0.9 \times 22.5 = 20.25$

27/2/2023
-2



AV
Firing

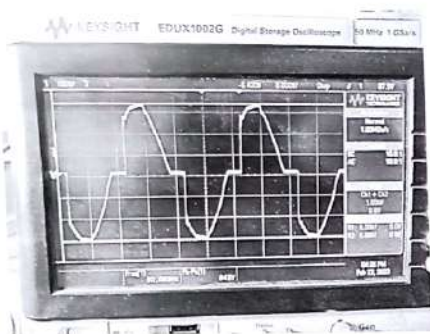

Reading-4
 $V_{out} = 192.4 \text{ V}$

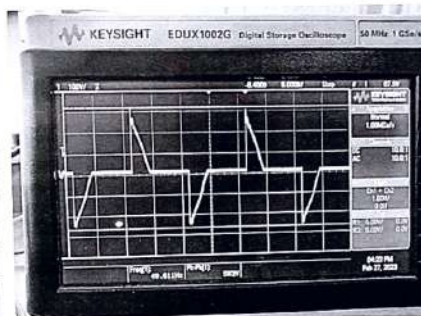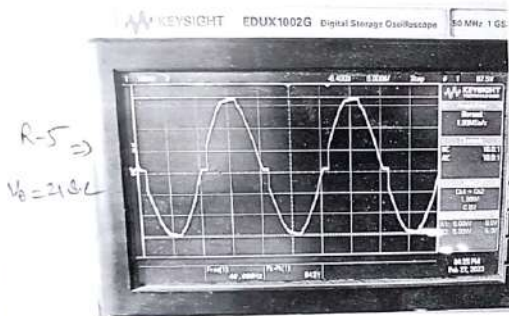

Reading-1
 $V_{out} = 45.9 \text{ V}$

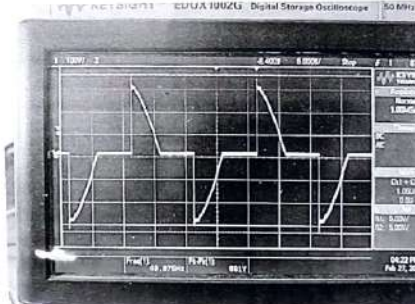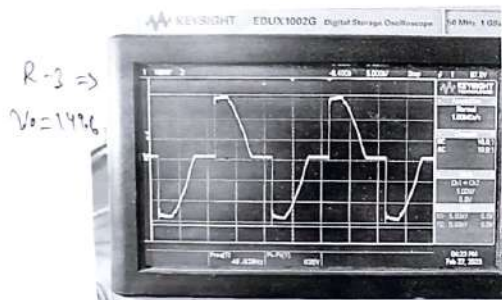

Reading-2
 $V_{out} = 94.1 \text{ V}$

Sample Calculation

Reading No. ③

$$16 \text{ divisions} = 360 = 2\pi$$

$$\alpha = \frac{360}{16} \times 3 = 67.5^\circ = 67.5 \times \frac{\pi}{180} = 1.17 \text{ radians}$$

$$V_{in} = 230 \text{ V}, \quad V_m = 230\sqrt{2} = 325.27 \text{ V}$$

$$\begin{aligned} V_{out} &= \frac{V_m}{\sqrt{2\pi}} \left((\pi - \alpha) + \frac{\sin 2\alpha}{2} \right)^{1/2} \\ &= \frac{325.27}{\sqrt{2\pi}} \left[(\pi - 1.17) + \frac{1}{2} \sin(2 \times 1.17) \right]^{1/2} \\ &= 198.11 \end{aligned}$$

$$\boxed{V_{out} = 198.11 \text{ V}}$$

Reading No. ⑤

$$\alpha = \frac{360}{16} \times 0.9 \times \frac{\pi}{180} = 0.353 \text{ radians}$$

$$V_{in} = 230 \text{ V}, \quad V_m = 230\sqrt{2} = 325.27 \text{ V}$$

$$\begin{aligned} V_{out} &= \frac{325.27}{\sqrt{2\pi}} \left[(\pi - 0.353) + \frac{1}{2} \sin(2 \times 0.353) \right]^{1/2} \\ &= 228.95 \end{aligned}$$

$$\boxed{V_{out} = 228.95}$$

Result Table


S.No.	Observed output Voltage (V)	Calculated Output Voltage (V)	Switching Angle (α) radians
1.	45.9	93.54	2.16
2.	94.1	154.24	1.65
3.	143.6	198.11	1.170
4.	192.4	219.51	0.785
5.	240.2	220.95	0.353

Theoretical & Obs. Voltage Vs. Switching Angle

Scales

X-axis: α unit = 0.2 rad

Y-axis: V unit = 20 V

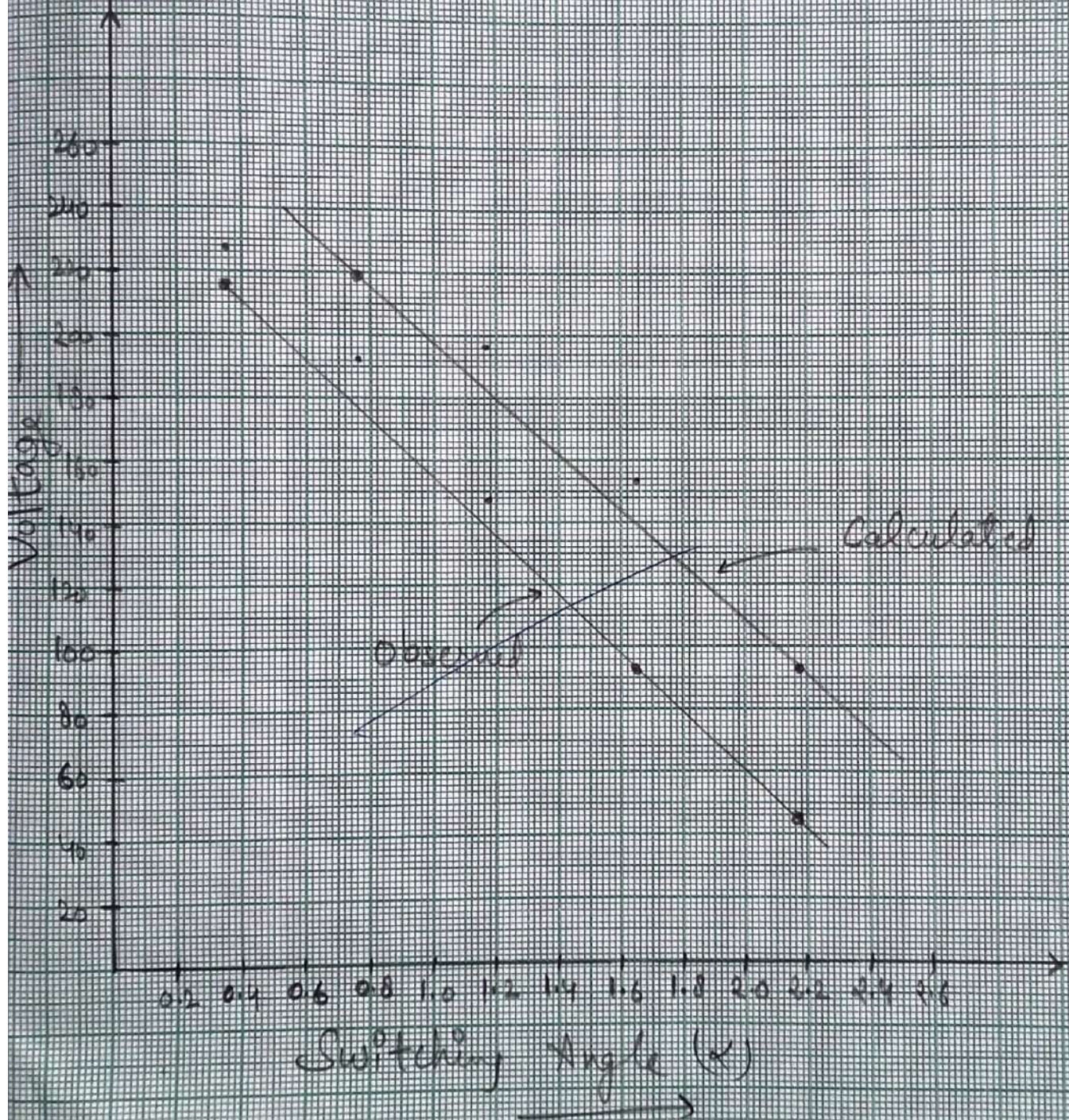

Discussion

Q) What are the advantages and disadvantages of a triac over SCR?

Ans: Advantage of TRIAC over SCR:

- (i) The TRIAC can be triggered by both +ve & -ve gate terminal.
- (ii) The TRIAC can control DC as well as AC Power.
- (iii) In TRIAC four different modes of operation are possible.


Disadvantage of TRIAC over SCR:

- (i) TRIAC is not reliable as compared to SCR.
- (ii) TRIAC is not suitable for D.C. application.
- (iii) It has very high switching delay.
- (iv) TRIAC has low rating as compared to SCR.

Q) Discuss the characteristics of a Diac.

Ans: A DIAC is a diode that conducts electric current only after its breakdown voltage (V_{BI}) has been reached. DIAC stands for "Diode for Alternating Current".

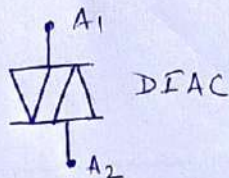A DIAC is a device which has two electrodes and is a member of thyristor family. DIAC are used in triggering of the resistors.



Q) What are maximum V_T , $\frac{di}{dt}$ and $\frac{dv}{dt}$ ratings of diac used?

Ans: $V_{max} = 230\sqrt{2} = 325.27\text{ V}$

Exp-7

(6)
P.
11/5/23

EEA-2970

GROUP NO.	03
CLASS S.NO.	14
SECTION	A2MB
NAME	PRANAY SINGH

EXPERIMENT NO.: 07

OBJECT: Speed control of Universal motor by SCR

DATE OF PERFORMING THE EXPERIMENT: 27/03/2023

DATE OF SUBMISSION OF REPORT: 03/04/2023

OTHER GROUP PARTNERS:

CLASS S.NO.	NAME
12	Gagan Pathak
13	Lakshmi Gupta
15	Mo. Arham
16	Prakhar Lahu

REMARK (If any by the teacher concerned):

EXP-05

PRANAY SINGH
21MEB448
CL2254

SUBJECT: Speed Control of Universal Motor (UM) by SCR.


(i) To study an RC triggering circuit for SCR.

(ii) To study the speed variation of UM using above triggering circuit for half wave control of ac supply voltage.

Apparatus Used:

No.	Equipment	Range	Make
1.	Hand Analog Tachometer	0-10000 rpm	Fuji Kogyo
2.	Universal Motor	230V	Tullu
3.	DSO (FDUX1002A)	50 MHz	Keysight
4.	Auto Transformer	0-230V	AE
5.	SCR	-	

Circuit Diagram:

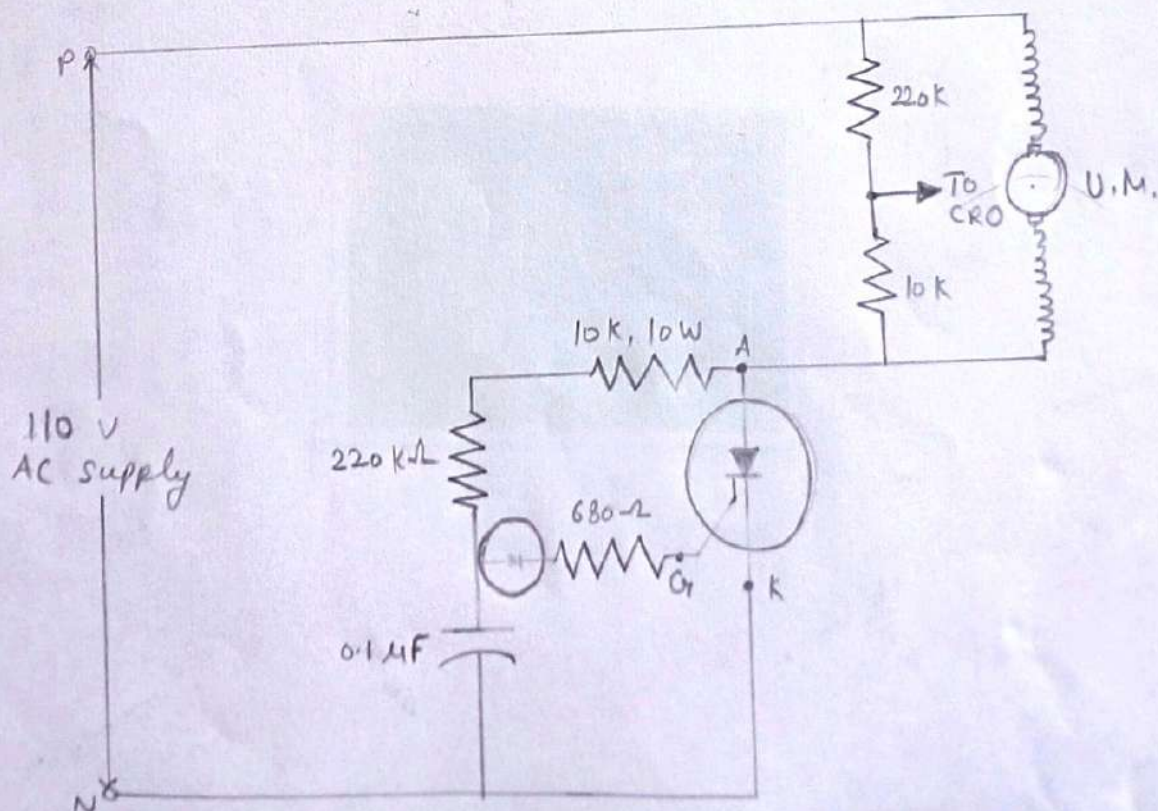





(I)



(II)



(III)




IV




(V)

Firing angle :

30V
 max limit = 5V
 min limit = 300 RPM

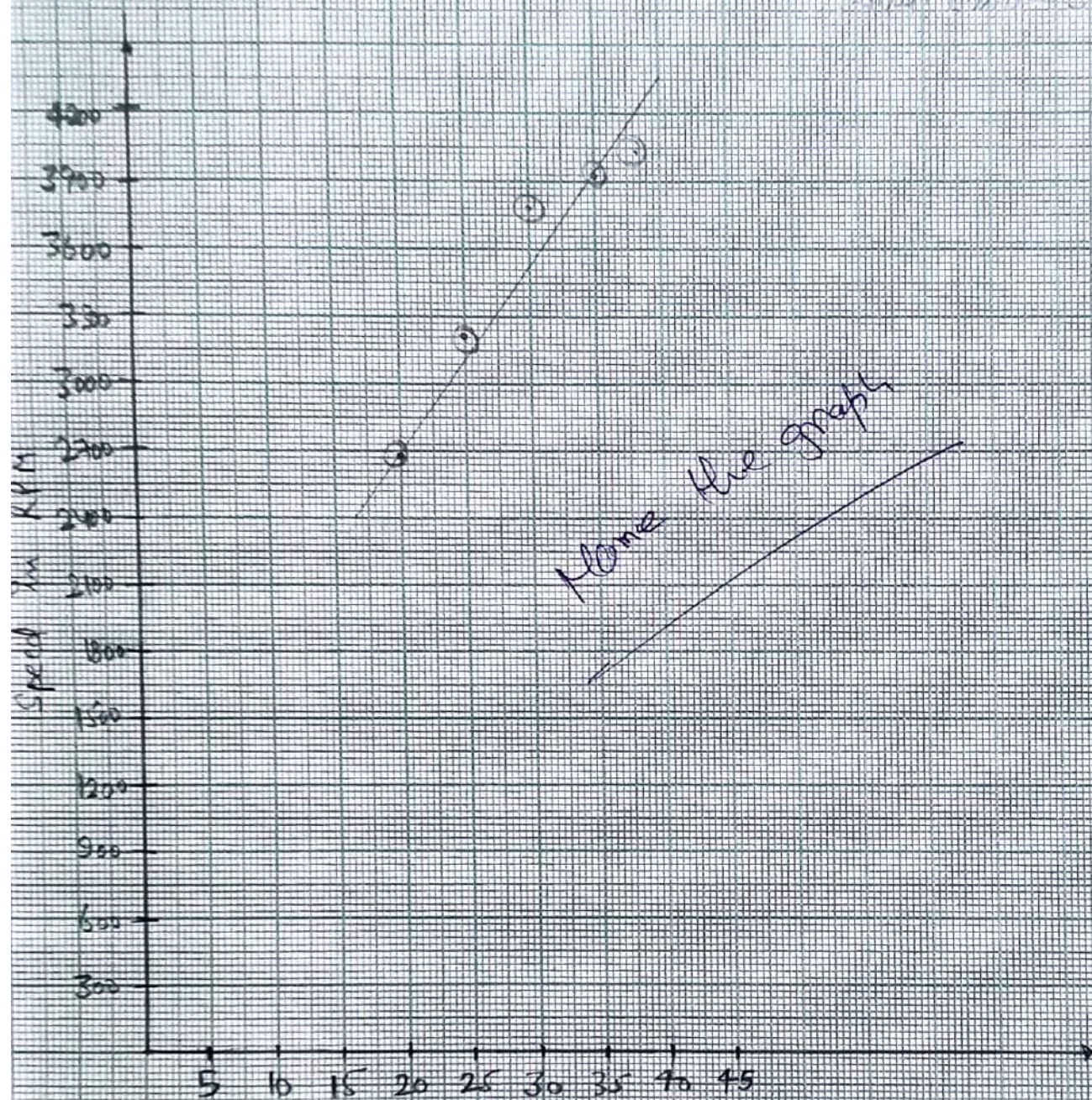

Voltage Xerox Motor →
 (V)

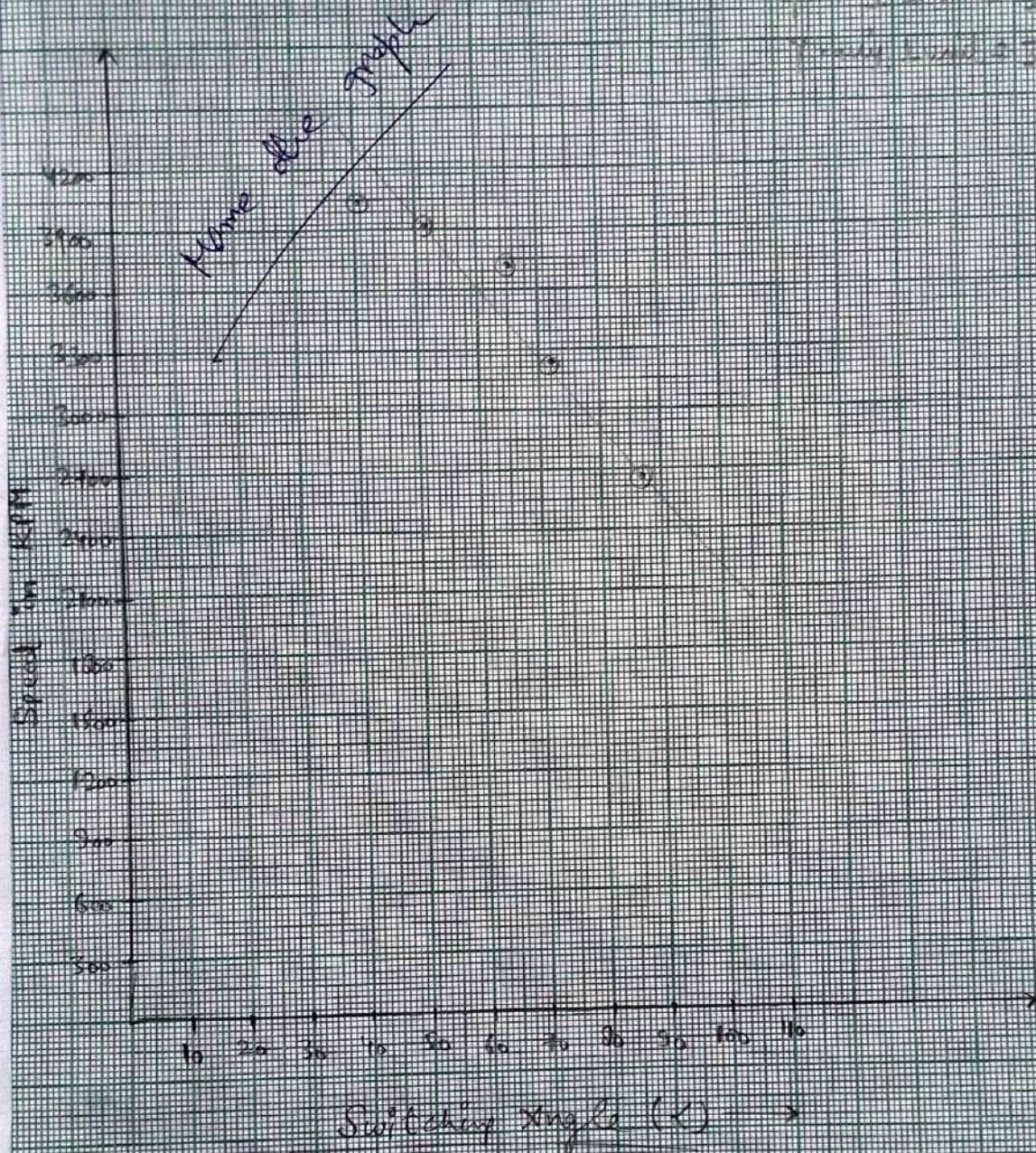

Graph
 x-axis limit = 100
 y-axis limit = 3800 rpm

Discussion

Q) Plot speed vs switching angle and comment on it.

Ans From the graph plotted b/w speed of the universal motor and switching angle, we can see that the speed and switching angle are inversely proportional to each other i.e. when the switching angle is increased the speed of motor decreases.

Q) Plot speed vs voltage and comment on it.

Ans From the graph plotted b/w speed of the universal motor and the supplied voltage, we can see the linearity b/w speed and voltage i.e. when the voltage across the motor is increased, the speed of the universal motor increases.

Speed of Motor $\propto$ Voltage across

Q) For an inductive circuit, explain how the load voltage changes even if switching angle did not change.

Ans:- Average output voltage is given by

$$V_{dc} = \frac{V_m}{2\pi} \int_0^{\pi} \sin \omega t \, d(\omega t)$$

$$V_{o(dc)} = \frac{V_m}{\pi} [1 + \cos \alpha], \quad V_m = I_s V_s$$

We can change the V_m supplied to the load by varying voltage across the variable diodes. Thus we can change the load voltage, even if the switching angle did not change by changing the value of gate current. Hence for an inductive circuit, by changing gate current, the load voltage changes even if the switching angle does not change.

Exp 08

7/2
10/4

EEA-2970

GROUP NO.	03
CLASS S.NO.	14
SECTION	A2MB
NAME	PRANAY SINGH

EXPERIMENT NO.: 08

OBJECT: Speed Control of dc motor by a phase controlled converter

DATE OF PERFORMING THE EXPERIMENT: 03/04/2023

DATE OF SUBMISSION OF REPORT: 10/04/2023

OTHER GROUP PARTNERS:

CLASS S.NO.	NAME
12	Dragan Pathak
13	Laksh Gupta
15	Ms. Arham
16	Pratihar Sahu


REMARK (If any by the teacher concerned):

OBJECT: Speed control of dc motor by a phase-controlled converter.


Apparatus Used:

S.No	Equipment Used	Range	Make
1.	Separately excited motor	1440 rpm, 0.5 HP 50 MHz	Speedway Tektronix
2.	DSO		A.E.
3.	Ammeter		
4.	Equipment kit	—	—
5.	Tachometer	1000 RPM	Teclock
6.	Auto Transformer	10 A, 270 V	A.E.

Circuit Diagram:

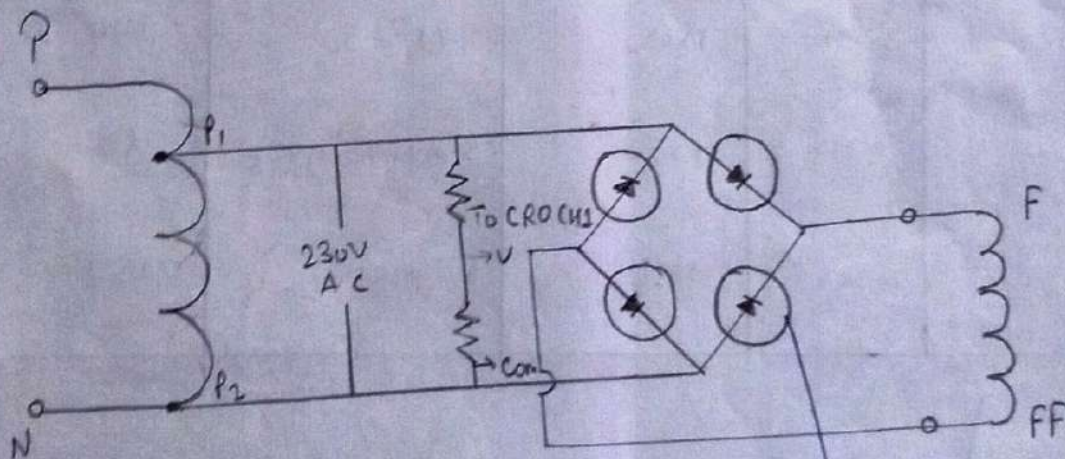

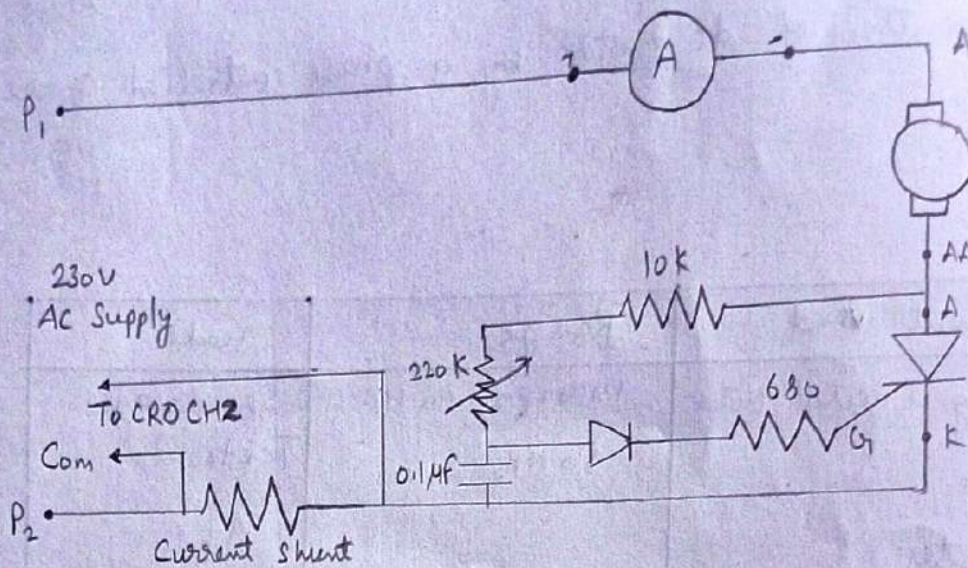Power Circuit for field winding of dc motor.






Power Circuit for armature of dc motor


Observation table:

S.No	Input Voltage (AC)	Armature Current (A)	Speed (r/min)	Triggering angle (α)	Armature Voltage (V)
1.	230	0.235	1760	$4.5 \times 18 = 81^\circ$	197
2.	230	0.225	1565	$5 \times 18 = 90^\circ$	177
3.	230	0.215	1330	$5.2 \times 18 = 93.6^\circ$	157
4.	230	0.205	1160	$5.8 \times 18 = 104.4^\circ$	137

3/4/2023

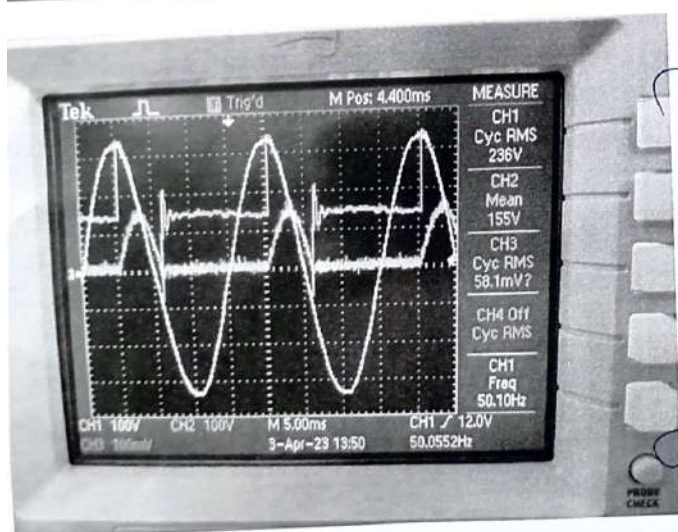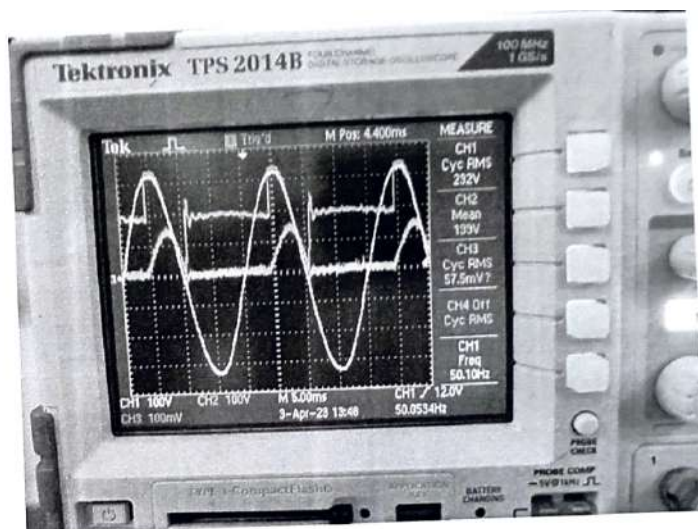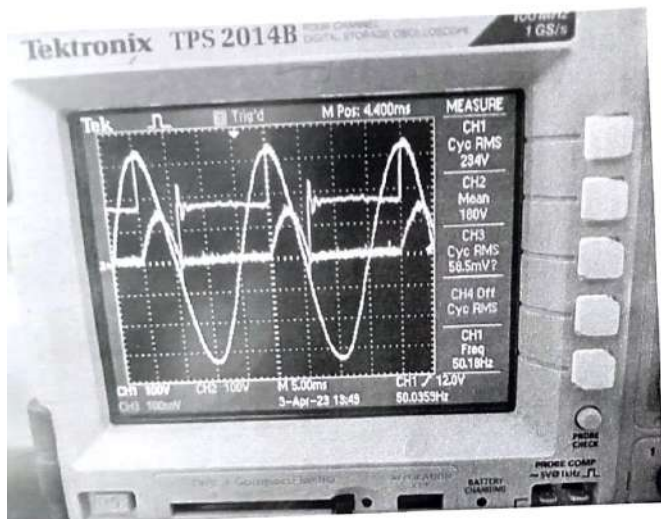

Capacitor

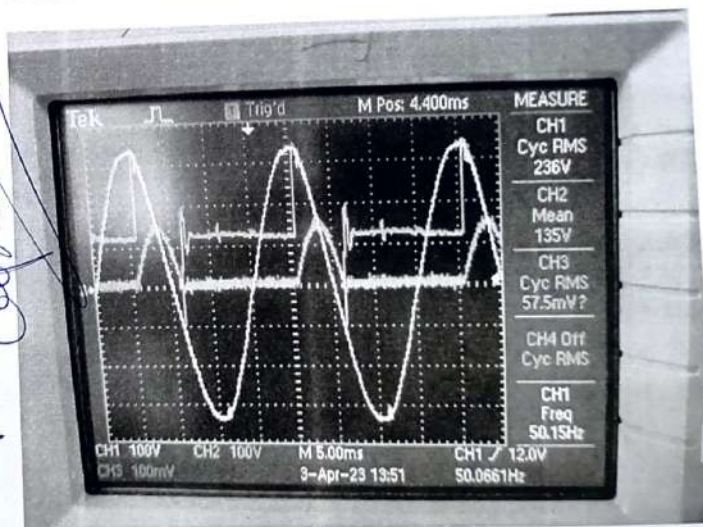


Speed vs triggering angle

Scale

1 grid square = 10

Trigger angle = 10°

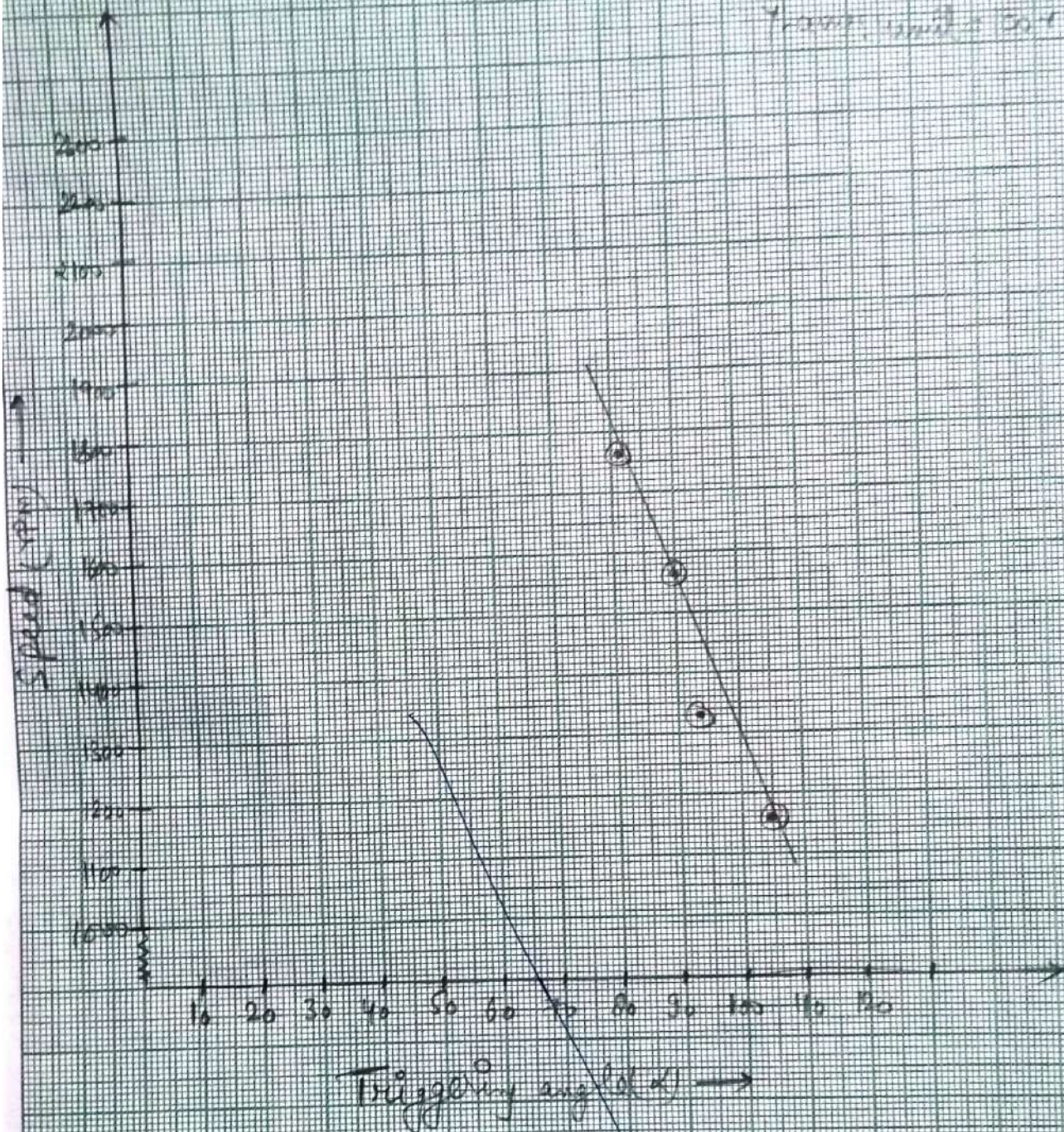

Calculation

No. of divisions in half wave = 10 divisions
Angle per division = $\frac{180}{10} = 18^\circ$

Triggering angle:

① No. of divisions = 4.5
Triggering angle (α) = $4.5 \times 18 = 81^\circ$

② No. of division = 5
Triggering angle (α) = $5 \times 18 = 90^\circ$

③ No. of division = 5.2
Triggering angle (α) = $5.2 \times 18 = 93.6^\circ$

④ No. of division = 5.8
Triggering angle (α) = 104.4°

Discussion:

Q Draw the graph of speed vs switching angle & comment.

Ans: After drawing the graph we can clearly conclude that when we increase triggering angle, there is a significant decrease in the speed of the motor.

Hence, it is clear that the speed of the D.C. motor can be controlled by using the controlled converter by adjusting the triggering angle (α).

$$239 \times 3.6 = 860.4$$

$$230 \times 0 = 0$$

$$\frac{0}{860.4} \times 100 = 0$$

$$238 \times 4.4 = 1047.2$$

$$230 \times 1.6 = 368$$

$$\frac{368}{1047.2} \times 100 = 35.14\%$$

$$238 \times 5 = 1190$$

$$230 \times 2 = 460$$

$$\frac{460}{1190} \times 100 = 38.66\%$$

$$238 \times 6 = 1428$$

$$230 \times 3.4 = 782$$

$$\frac{782}{1428} \times 100 = 54.76\%$$

$$238 \times 7.2 = 1713.6$$

$$230 \times 4.6 = 1058$$

$$\frac{1058}{1713.6} \times 100 = 61.74\%$$

$$238 \times 9.2 = 2189.6$$

$$230 \times 6.2 = 1426$$

$$\frac{1426}{2189.6} \times 100 = 65.13\%$$

$$238 \times 10.6 = 2522.8$$

$$230 \times 7.6 = 1748$$

$$\frac{1748}{2522.8} \times 100 = 69.29\%$$